

Coulombkraft:

$$\vec{F}_C = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{|\vec{r}|^2} \cdot \frac{\vec{r}}{|\vec{r}|}$$

$$|\vec{F}_C| = \frac{q_1 q_2}{4\pi\epsilon_0 r^2}$$

Potential:

$$F_c = - \frac{\partial E_{\text{pot}}}{\partial r}$$

$$E_{\text{pot}}(r) = \frac{q_1 q_2}{4\pi\epsilon_0 r}$$

Stokes'sche Reibung:

$$\vec{F}_s = -b_s |\vec{v}| \frac{\vec{v}}{|\vec{v}|}$$

Temperaturabhängigkeit des spez. Widerstands:

$$\rho(T) = \rho_0 (1 + \alpha (T - T_0)) \quad \alpha = \text{Temp. Koeffizient}$$

$$\text{Spannungsquellen } U_B = \frac{\partial W}{\partial Q} \quad \rho_{el} = \frac{\partial W}{\partial t} = \frac{\partial W}{\partial Q} \frac{\partial Q}{\partial t} = U_B I = \frac{U_B^2}{R}$$

$$U_{B, \text{ges}} = \sum_{i=1}^N U_{B_i}, \quad \text{unverzweigte Gleichstromreihe} \quad U_B - U_R = U_B - IR = 0$$

$$U_B = RI$$

$$\text{Batterie mit Innen-R: } U_B - I R_{\text{innen}} - IR = 0 \quad U_{\text{Klemm}} = U_B - I R_{\text{innen}}$$

$$R \text{ in Reihe: } U - I \sum_{i=1}^N R_i = 0$$

$$\text{Potential / Spannungsdiff. im Stromkreis } U_1 - U_2 = IR \quad \text{auch Spannungsabfall an } R$$

Verzweigte Stromkreise, Parallelschaltung von Widerständen:

$$U = I_1 R_1 = I_2 R_2 = I_3 R_3 \Rightarrow \text{Kirchhoff}$$

$$I = I_1 + I_2 + I_3 = U \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \quad R_{eq} = \left(\sum_{i=1}^N \frac{1}{R_i} \right)^{-1} \quad U = I R_{eq}$$

$$\text{Kondensatoren } |\vec{E}| = \frac{U}{L} \quad U = U_B \quad Q = CU \quad C = \epsilon_0 \frac{A}{d}$$

$$\text{Energie } E_c = \frac{1}{2} C U_0^2, \quad \text{parallel: } U = U_B \quad q_1 = C_1 U, \quad q_2 = C_2 U,$$

$$\text{Reihe: } U_1 = \frac{q}{C_1}, \quad U = U_1 + U_2 = \dots = q \left(\frac{1}{C_1} + \frac{1}{C_2} \right), \quad C_{eq} = \frac{Q}{U}, \quad Q = \sum_{i=1}^N q_i, \quad C_{eq} = \sum_{i=1}^N C_i$$

$$U = \frac{Q}{C_{eq}}, \quad C_{eq} = \text{Gesamtkapazität} = \left(\sum_{i=1}^N \frac{1}{C_i} \right)^{-1}$$

$$\text{Der RC-Kreis } U_0 - IR - \frac{Q}{C} = 0 \quad Q_0 = CU_0 \quad I = \frac{\partial Q}{\partial t}$$

$$\text{Entladung: } Q(t) = Q_0 \exp\left(-\frac{t}{\tau_c}\right) \quad \tau_c = RC \quad Q_{\tau_c} = \frac{Q_0}{e} \quad t_{c, \frac{1}{2}} = \ln(2) \tau_c$$

$$U(t) = U_0 \exp\left(-\frac{t}{\tau_c}\right), \quad I(t) = -I_0 \exp\left(-\frac{t}{\tau_c}\right), \quad I_0 = \frac{U_0}{R}$$

$$\text{Aufladung wenn } Q(0)=0: \quad Q(t) = (U_0(1 - \exp(-\frac{t}{\tau_c})) = Q_0(1 - \exp(-\frac{t}{\tau_c}))$$

$$U_c(t) = \frac{Q_0}{C} (1 - \exp(-\frac{t}{\tau_c})) = U_0 (1 - \exp(-\frac{t}{\tau_c})), \quad I(t) = I_0 e^{-t/\tau_c}$$

$$\text{Induktivität } U = -L \frac{\partial I}{\partial t} = -U_L \quad L = \mu_0 \frac{N^2 A}{l}$$

$$\text{R-L-Kreis: } U_0 - IR - L \frac{\partial I}{\partial t} = 0$$

$$\text{Einschalten der Spule: } I(t) = \frac{U_0}{R} (1 - \exp(-\frac{t}{\tau_L})) = I_0 (1 - \exp(-t/\tau_L))$$

$$\text{Zeitkonstante: } \tau_L = \frac{L}{R} \quad I_0 = \frac{U_0}{R}$$

$$\text{Spannungsabfall an Spule: } U_L(t) = U_0 (1 - \exp(-\frac{t}{\tau_L})) = U_0 (1 - e^{-t/\tau_L})$$

$$\text{Induktionsspannung: } U_L(t) = U_0 - U_R(t) = U_0 e^{-t/\tau_L}$$

$$\text{Ausschalten: } I = \frac{U_0}{R} e^{-t/\tau_L} = I_0 e^{-t/\tau_L}, \quad U_L(t) = -U_0 e^{-t/\tau_L}$$

$U(r) := \text{el. Potential [V]}$

$$U(r) = \frac{E_{\text{pot}}(r)}{q_2} = \frac{q_1}{4\pi\epsilon_0 r}$$

mit n -Punktladungen:

$$U_{p, \text{ges}} = \sum_{i=1}^N U_i = \frac{1}{4\pi\epsilon_0} \sum_{i=1}^N \frac{q_i}{r_i}$$

$$U_{pp}(x) = U_{\text{max}} \frac{x}{L}$$

$$\Delta E_{\text{pot}} = q U_{\text{max}} = q \Delta U$$

$$E_{\text{pot}}(x) = -e U_{pp}(x) = -e U_{\text{max}} \frac{x}{L} = -e U \frac{x}{L}$$

$$F_x(x) = - \frac{\partial E_{\text{pot}}(x)}{\partial x} = \frac{eU}{L}$$

$$a_x = \frac{F_x}{m_e} = \frac{eU}{m_e L} \quad v_x = \sqrt{2 a_x L} = \sqrt{\frac{2eU}{m_e}}$$

Ablenkung vom Kondensator

$$\vec{v} = \begin{pmatrix} v_x \\ v_y \end{pmatrix} = \begin{pmatrix} \frac{e U_{\text{max}}}{m_e L} \\ v_y \end{pmatrix}$$

Das elektrische Feld

$$\vec{F}_c(\vec{r}) = q_2 \vec{E}_c(\vec{r}), \quad \vec{E}_c(\vec{r}) = \frac{1}{4\pi\epsilon_0} \frac{q_1}{|\vec{r}|^2} \frac{\vec{r}}{|\vec{r}|}$$

$$|\vec{E}| = \frac{U}{L} \quad \vec{F} = q \vec{E}, \quad F_x(x) = -e |\vec{E}|$$

(Kondensator)

Elektrischer Strom

$$I = \frac{\partial Q}{\partial t} \quad Q = \int_{t_1}^{t_2} I dt$$

$$I = \frac{-e v}{\Delta x} = \frac{q v}{\Delta x}$$

Ladungsträgerdichte $n = \frac{N}{V}$ ← freie Ladungsträger
← Volumen

$$\rho_q = n q = \frac{N}{V} q := \text{Ladungsdichte}$$

$$n_{el} = \frac{Q}{C}$$

$$I = n_{el} (-e) v \cdot A = j A$$

$$j := n_{el} (-e) v := \text{Stromdichte} \left[\frac{A}{m^2} \right]$$

$$|\vec{E}_{el}| = \frac{e U}{L}$$

$$\text{Driftgeschw.} = v_{max} = v_D$$

$$v_D = -\frac{I}{n_{el} e A} = -\frac{j}{n_{el} e}$$

$$I = \frac{U}{R}$$

Elektrischer Strom u. E.-Erhaltung:

$$\Delta E_{pot} = -e (U_2 - U_1) = -e U$$

$$\Delta E_{kin} = E_{kin,2} - E_{kin,1} = \frac{1}{2} m v_D^2 - \frac{1}{2} m v_0^2 = 0$$

$$\frac{\partial (\Delta E_{pot, ges})}{\partial t} = \frac{\partial Q}{\partial t} U = I U$$

El. Leistung $P_{el} = U \cdot I$ Einheit [W] = [Js]

Ohmscher Widerstand:

$$R = \frac{U}{I} \quad P = U I = I^2 R = \frac{U^2}{R}$$

Der Spezifische Widerstand $\left[\frac{\Omega \cdot m}{m} \right]$

$$R = \rho \frac{L}{A} \Rightarrow \rho = R \frac{A}{L} \quad \sigma = \frac{1}{\rho} \text{ spez. Leitfähigkeit}$$

$$\vec{E} = \rho \vec{j}$$

$$\rho = \frac{|\vec{E}|}{|\vec{j}|} = \frac{U/L}{I/A} = R \frac{A}{L}$$

Drude-Modell:

$$a = \frac{F_{el}}{m_e} = \frac{e |\vec{E}|}{m_e} \quad |\vec{v}| = a \tau = \frac{e |\vec{E}| \tau}{m_e} \quad \tau = \frac{m_e}{e^2 n_{el} T}$$

τ Zeit vor Stoß $|\vec{v}| = \frac{|\vec{j}|}{n_{el} e} \quad |\vec{E}| = \left(\frac{m_e}{e^2 n_{el} T} \right) |\vec{j}|$

Selbstinduktion, Ausschalten: $I(t) = I_0 e^{-t/\tau_L} = \frac{U}{R_1} e^{-\frac{R_2}{L} t}$

$$U_{L,0} = U \frac{R_2}{R_1} \quad \tau_L = \frac{L}{R_2} \quad U_L(t) = -U \frac{R_2}{R_1} e^{-\frac{R_2}{L} t}$$

Spule als E-Speicher: $E_{pot} = \frac{1}{2} R I_0^2 \frac{L}{R} = \frac{1}{2} L I_0^2$

Wechselstrom: $u(t) = U_0 \cos(\omega t) = U_0 \cos(2\pi f t)$

$$i(t) = I_0 \cos(\omega t + \varphi) = I_0 \cos(2\pi f t + \varphi)$$

$$\vec{u}(t) = U_0 e^{i(\omega t)}, \quad \vec{i}(t) = I_0 e^{i(\omega t + \varphi)}$$

R in Wechselstrom:

$$I_R(t) = \frac{u(t)}{R} = \frac{U_0}{R} \cos(\omega t) = I_0 \cos(\omega t) \quad I_0 = \frac{U_0}{R} = \frac{U_0}{|Z_R|}$$

C in Wechselstrom:

$$u(t) = U_0 \cos(\omega t) \quad Q(t) = (U_0 \cos(\omega t)) I_C = - (U_0 \omega \sin(\omega t)) = I_0 \cos(\omega t + \frac{\pi}{2})$$

$$I_0 = U_0 \omega C = \frac{U_0}{|Z_C|} \quad |Z_C| = \frac{1}{\omega C}$$

L in Wechselstrom:

$$\frac{\partial I_L}{\partial t} = \frac{U_0}{L} \cos(\omega t) \quad I_L(t) = I_0 \sin(\omega t) = I_0 \cos(\omega t - \frac{\pi}{2})$$

$$I_0 = \frac{U_0}{\omega L} = \frac{U_0}{|Z_L|} \quad |Z_L| = \omega L$$

Impedanz $\alpha(t) = U_0 e^{i(\omega t)}, \quad \vec{i}(t) = i \omega C \alpha(t)$

$$Z_C = \frac{1}{i \omega C} \quad z_C = |Z_C| e^{-i\varphi_C} \quad \varphi_C = \frac{\pi}{2} \quad \vec{i}(t) = I_0 e^{i(\omega t + \varphi_C)}$$

$$Z_L = i \omega L = |Z_L| e^{-i\varphi_L} \quad \varphi_L = -\frac{\pi}{2} \quad \text{Re}(\vec{i}(t)) = I_0 \cos(\omega t + \varphi_C)$$

$$Z_R = R = |Z_R| e^{-i\varphi_R} = |Z_R| e^{-i\varphi_R} \quad \varphi_R = 0$$

$$Z_{eq} = \sum_{i=1}^n Z_i \quad (\text{Reihe}), \quad Z_{eq} = \left(\sum_{i=1}^n \frac{1}{Z_i} \right)^{-1} \quad (\text{Parallel})$$

Kombinationen im Wechselstromkreis:

Ohmscher Spannungsteiler $\alpha(t) = U_0 e^{i \omega t}$

$$\vec{i}(t) = \frac{U_0}{R_{eq}} e^{i \omega t} = \frac{U_0}{R_1 + R_2} e^{i \omega t}$$

$$\vec{u}_1(t) = \vec{i}(t) R_1 = \frac{R_1}{R_1 + R_2} U_0 e^{i \omega t} = \frac{R_1}{R_1 + R_2} \vec{u}(t)$$

$$U_2 = \frac{R_2}{R_{eq}} U_0 \quad R_{eq} = Z_{eq} = R_1 + R_2$$

$$\int_P dU = \epsilon_0 \oint \vec{E} \cdot d\vec{A} = \epsilon_0 \int \vec{\nabla} \cdot \vec{E} dV$$

$$\vec{\nabla} \cdot \vec{E} = \frac{\rho}{\epsilon_0}$$